





Ugd verandert door audio signaal, Cgd heeft dus invloed.

Uds verandert door audio signaal, Cds heeft dus invloed.

Ugd, Uds bijna constant, Cgd, Cds geminimaliseerd.

Inwendige impedantie veel groter => betere stroom bron.

Stroombron niet goed genoeg met grote spanningen.

U [V]	I [mA]	R [Ohm]
40	3.05	583.3
30	3.03	625
20	3.02	500
10	3.00	500
5	2.99	-

U [V]	I [mA]	R [Ohm]
40	3.00	-
30	3.00	-
20	3.00	-
10	3.00	-
5	3.00	-

Ids [mA]	P [Ohm]
1.12	1030
1.50	743
2.00	538
3.00	343
4.00	247
5.00	190
6.00	154
7.00	129
8.00	110
9.00	95
10.00	84

