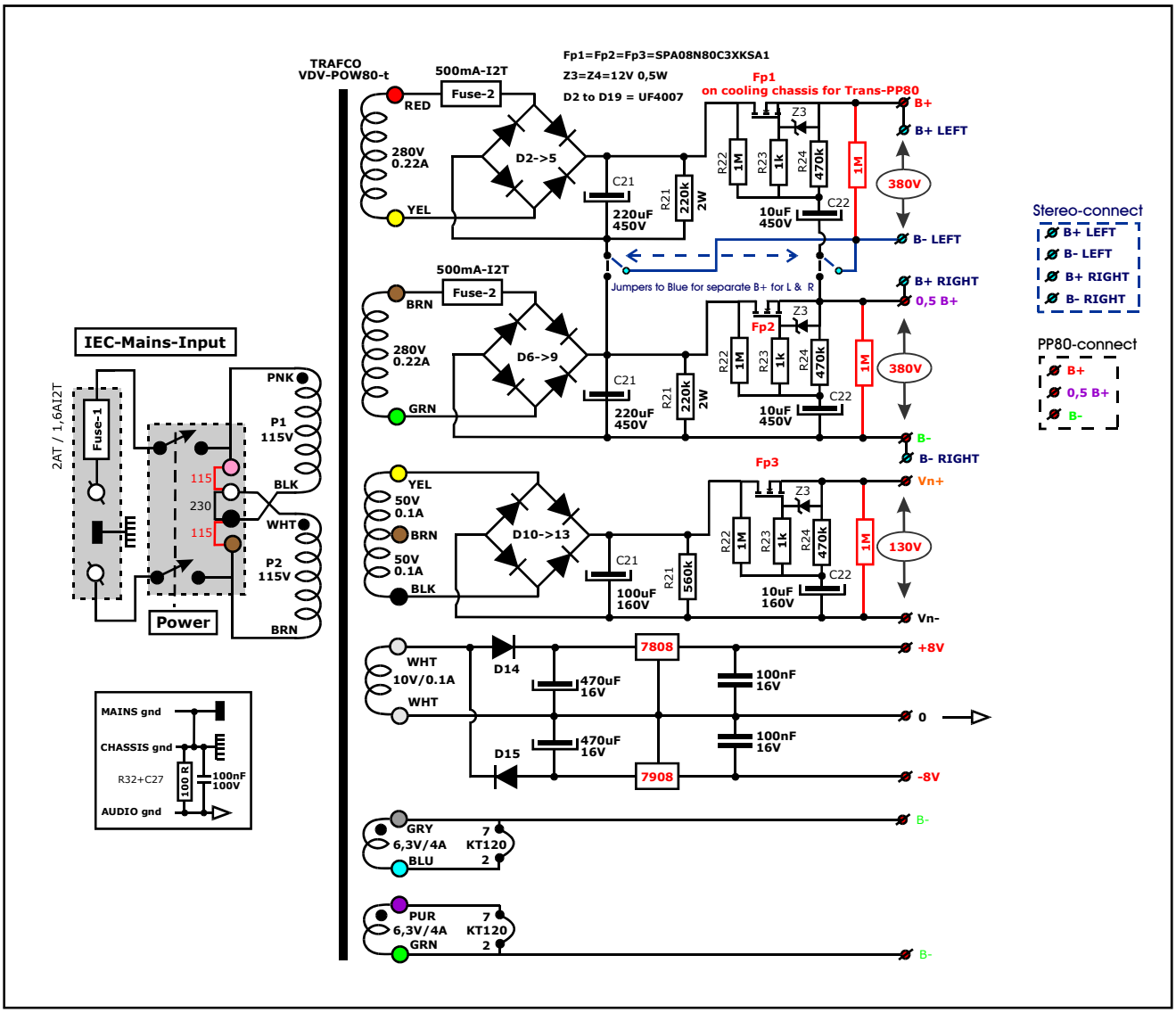Example of power supply for 80 Watt Trans-pp amplifier